

ECE 362 Homework 1 Solutions

1.1 2.1 Function is true for binary 0101010101 and 1010101010

$\Sigma(341, 682)$

2.2

e1	x1	e2	x2	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	X
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	X
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

1.2 2.3

x	y	z	fa	fb
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	0	1
1	1	0	1	1
1	1	1	0	0

$$\begin{aligned}
 fa &= x'y'z' + x'yz' + xyz' \quad (\text{canonical sum}) \\
 &= (x+y+z')(x+y'+z)(x'+y+z)(x'+y'+z')(x'+y'+z') \quad (\text{canonical product})
 \end{aligned}$$

$$\begin{aligned}
 fb &= x'y'z' + x'yz' + xy'z' + xy'z + xyz' \quad (\text{canonical sum}) \\
 &= (x+y+z')(x+y'+z)(x'+y'+z') \quad (\text{canonical product})
 \end{aligned}$$

2.4

$$\begin{aligned}
 &b^2c + acd' + a^2c + eb' + e(a+c)(a'+d') \\
 &b^2(c+e) + c(ad'+a') + e(a+c)(ad)' \\
 &b^2(c+e) + c(a'+d') + e(a+c)(ad)' \\
 &b^2(c+e) + c(ad)'+ e(a+c)(ad)' \\
 &b^2(c+e) + (c+ea+ec)(ad)' \\
 &b^2(c+e) + (c+ea)(ad)'
 \end{aligned}$$

1.3 2.6 a Prove by expanding to canonical sum and showing that they are equal

$$\begin{aligned} & ab' + bc' + ca' \\ &= ab'c + ab'c' + abc' + a'bc' + a'bc + a'b'c \end{aligned}$$

$$\begin{aligned} & a'b + b'c + c'a \\ &= a'bc + a'bc' + ab'c + a'b'c + abc' + ab'c' \end{aligned}$$

b Show by derivation

$$\begin{aligned} & ab + a'c + bcd \\ & abc + abc' + a'bc + a'b'c + bcd \\ & bc(a+a') + abc' + a'b'c + bcd \\ & bc + abc' + a'b'c + \cancel{bcd} \\ & bc(a+a') + abc' + a'b'c \\ & abc + abc' + a'bc + a'b'c \\ & ab + a'c \end{aligned}$$

2.7 a $f' = (a+bc)'$
 $= a'(bc)'$
 $= a'(b' + c')$
 $= a'b' + a'c'$

$$\begin{aligned} ff' &= (a+bc)(a'b'+a'c') \\ &= \cancel{aa'b'} + \cancel{aa'e^2} + \cancel{a'bb'e} + a'bee^2 \\ &= 0 \end{aligned}$$

b $f' = ((a+b)(a'c+d))'$
 $= (a+b)' + (a'c+d)'$
 $= a'b' + (a'c)'d'$
 $= a'b' + (a+c')d'$
 $= a'b' + ad' + c'd'$

$$\begin{aligned} ff' &= (a+b)(a'c+d)(a'b'+ad'+c'd') \\ &= (\cancel{aa'e+ad+a'bc+bd})(a'b'+ad'+c'd') \\ &= \cancel{aa'b'd} + \cancel{add^2} + \cancel{ae'dd^2} + a'bb'e + \cancel{aa'bed^2} + a'bee'd^2 + a'bb'd + \cancel{abdd^2} + \cancel{be'dd^2} \\ &= 0 \end{aligned}$$

c $f' = (ab+b'c+ca'd)'$
 $= (ab)'(b'c)'(ca'd)'$
 $= (a'+b')(b+c')(c'+a+d')$
 $= (a'b+a'c'+\cancel{bb^2}+b'c')(c'+a+d')$
 $= \cancel{a^2be^2} + \cancel{aa^2b} + a'bd' + a'c' + \cancel{aa^2e^2} + \cancel{a^2e^2d^2} + b'c' + \cancel{ab^2e^2} + \cancel{b^2e^2d^2}$
(absorbition)
 $= a'bd' + a'c' + b'c'$

$$\begin{aligned} ff' &= (ab+b'c+ca'd)(a'bd'+a'c'+b'c') \\ &= \cancel{aa^2bd^2} + \cancel{aa^2be^2} + \cancel{abb^2e^2} + \cancel{a'bb^2ed^2} + \cancel{a^2b^2ee^2} + \cancel{b^2ee^2} + \cancel{a^2bedd^2} + \cancel{a^2ee^2d} + \cancel{a^2b^2ee^2d} \\ &= 0 \end{aligned}$$

1.4 2.9

a	z1	z2	z3	w
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	1
	1	0	0	0
	1	0	1	1
	1	1	0	1
	1	1	1	1

b $\Sigma(3, 5, 6, 7)$

c $w = z_1z_2 + z_1z_3 + z_2z_3$

2.11 a $f = x'y + xy'$

b $(x \oplus y) \oplus z$

$$\begin{aligned}
 & (x'y + xy') \oplus z \\
 & (x'y + xy')'z + (x'y + xy')z' \\
 & (x'y)'(xy')'z + x'yz' + xy'z' \\
 & (x+y')(x'+y)z + x'yz' + xy'z' \\
 & (\cancel{xx}^2 + xy + x'y' + \cancel{yy}^2)z + x'yz' + xy'z' \\
 & xyz + x'y'z + x'yz' + xy'z' \\
 & x'(y'z + yz') + x(yz + y'z') \\
 & x'(y \oplus z) + x((yz)'(y'z')')' \\
 & x'(y \oplus z) + x((y'+z')(y+z))' \\
 & x'(y \oplus z) + x(\cancel{yy}^2 + y'z + yz' + \cancel{zz}^2)' \\
 & x'(y \oplus z) + x(y \oplus z)' \\
 & x \oplus (y \oplus z)
 \end{aligned}$$

c If $x \oplus y = z$,

$$x \oplus z = x \oplus (x \oplus y) = (x \oplus x) \oplus y = 0 \oplus y = y$$

$$x \oplus y \oplus z = x \oplus y \oplus (x \oplus y) = (x \oplus x) \oplus (y \oplus y) = 0 \oplus 0 = 0$$

d If $xy = 0$,

$$\begin{aligned}
 & x \oplus y \\
 & x'y + xy' \\
 & ((x'y)'(xy')')' \\
 & ((x+y')(x'+y))' \\
 & (\cancel{xx}^2 + xy + x'y' + \cancel{yy}^2)' \\
 & (0 + x'y')' \\
 & (x'y')' \\
 & x + y
 \end{aligned}$$

e $(a+b) \oplus (a+c)$
 $(a+b)'(a+c) + (a+b)(a+c)'$
 $a'b'(a+c) + (a+b)a'c'$
 $aa'b' + a'b'c + aa'e' + a'bc'$
 $a'(b'c+bc')$
 $a'(b \oplus c)$

f $x \oplus y \oplus xy$
 $x'(y \oplus xy) + x(y \oplus xy)'$
 $x'(y'xy + y(xy)') + x(y'xy + y(xy)')$
 $x'y(x'+y') + x(y'+xy)$
 $x'y + x'yy' + xy' + xy$
 $x + y$

$x \oplus x'y$
 $x'x'y + x(x'y)'$
 $x'y + x(x+y')$
 $x'y + x + xy'$
 $x + y$


1.5 3.1 a $f = ((c+x+y2)y1(xy2)')'$

Using DeMorgan's,

$$f = (c+x+y2)' + y1' + xy2$$

$$= c'x'y2' + y1' + xy2$$

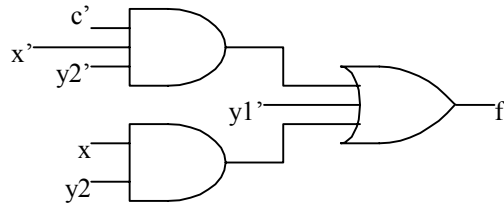
b There are several ways of interpreting this problem. Here is one possible solution:



c For the schematic in part b,

$$f = c'x'y2' + y1' + xy2$$

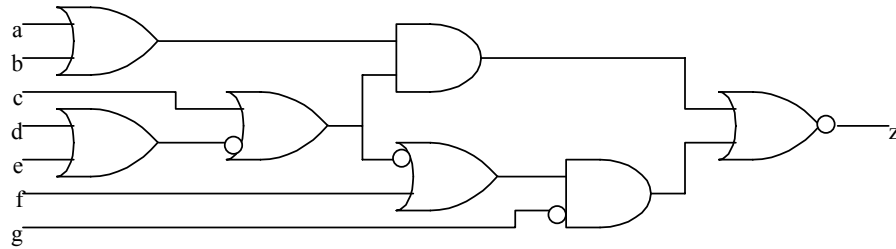- 3.2 a There are several ways of interpreting this problem. Here is one possible solution:



b $z = ((a'b')'(c'(d'e')'))'(((c'(d'e')')'f')'g)'$

c $(a'b'+c'(d'e'))((c'(d'e')')'f'+g)$
 $(a'b'+c'(d+e))((c+d'e')f'+g)$
 $(a'b'+c'd+c'e)(cf'+d'e'f'+g)$
 $a'b'cf' + a'b'd'e'f' + a'b'g + ce'df' + e'dd'e'f' + c'dg + ce'ef' + e'd'ee'f' + c'eg$
 $a'b'cf' + a'b'd'e'f' + a'b'g + c'dg + c'eg$

d $((a'+b')+(c'+(d'+e')'))' + (((c'+(d'+e')')'f')'+g)'$


e ... skipping lots of algebra ...

$$a'c' + a'de + b'c' + b'de + cd'g + ce'g + f'g$$

Take the dual:

$$(a'+c')(a'+d+e)(b'+c')(b'+d+e)(c+d'+g)(c+e'+g)(f'+g)$$

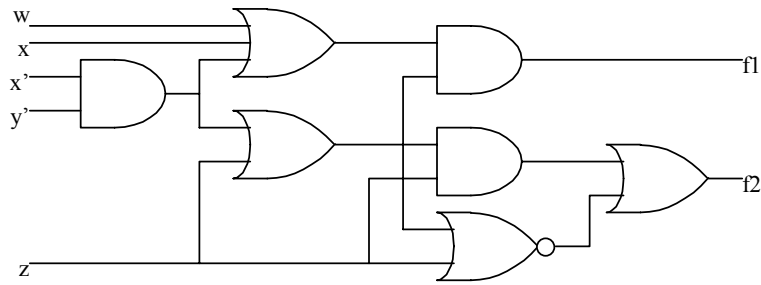1.6 3.5 There are several ways of interpreting this problem. Here is one possible solution:



$$f1 = (w+x+x'y')(z+x'y')$$

$$\begin{aligned} f2 &= ((x+y)z) \oplus z \\ &= ((x+y)z)z' + (x'y'z)z \\ &= ((x+y)z)z' + x'y'z + z \\ &= z + (z+(x+y)z')' \\ &= z + (x+y)z' \\ &= x + y + z \end{aligned}$$

3.7 a $(x_1x_2+x_3)(x_2+x_4+x_5) + x_5 + x_3x_4$

b $x_1x_2 + x_2x_3 + x_3x_4 + x_3x_5 + x_5 + x_3x_4$
 $x_1x_2 + x_2x_3 + x_3x_4 + x_5$